




GO GREEN

Eco Friendly, Energy Saving Street Light

AMIT KRISHNA A

Exhibit 1: Automatic Light Detector

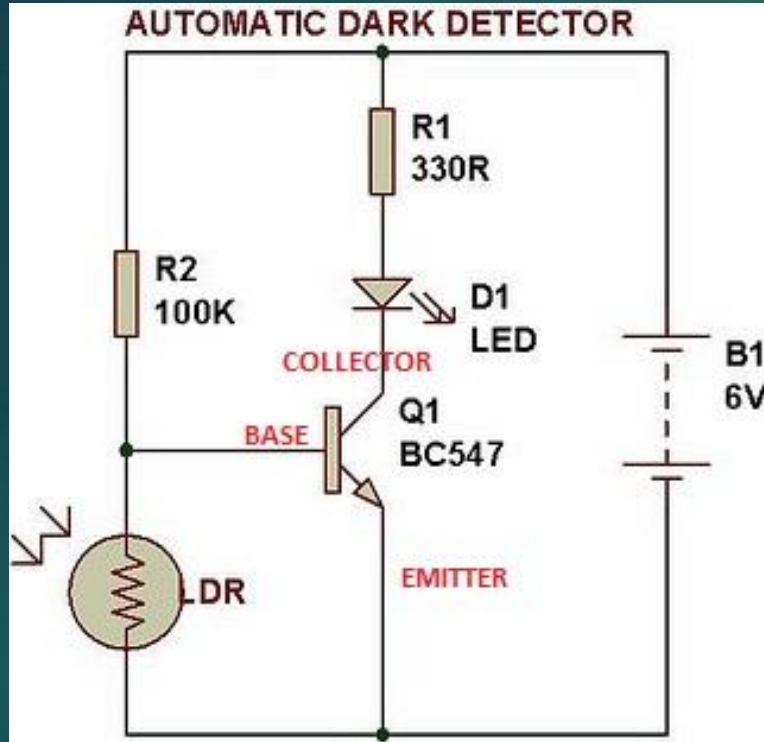

Voltage between BASE &
EMITTER = $(B1 * LDR) / (LDR + R2)$

- Light Dependent Resistor (LDR):
 - Resistance is HIGH when it is DARK
 - Resistance is LOW when it is BRIGHT
- Light Emitting Diode (LED) is the STREET LIGHT
- Transistor is the SWITCH
 - Voltage between BASE & EMITTER collector > 0.7V, SWITCH IS ON, Current flows through LED, Street Light is ON
 - Voltage between BASE & EMITTER collector < 0.7V, SWITCH IS OFF, No current flows through LED, Street Light is OFF

ADVANTAGES:

Street Light is ON only when it is dark. Reduces wastage of Electricity

Automatic ON/OFF: No Electrician required to switch the light ON and OFF

Exhibit 2: Infra Red Controlled Light Source (“Virtual Sun”)



GO GREEN

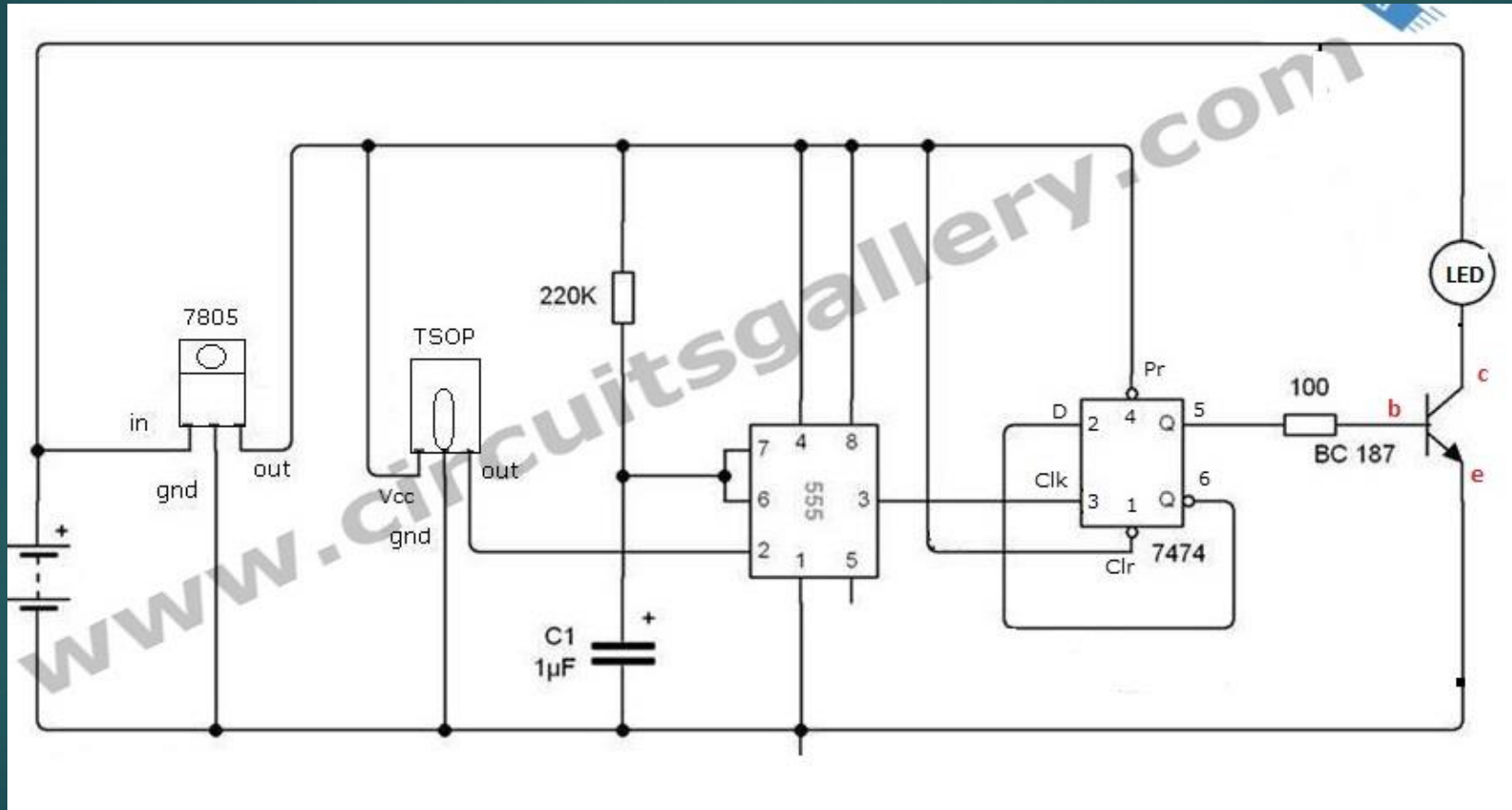


Exhibit 2: Infra Red Controlled Light Source (“Virtual Sun”)



- ▶ 7805 – Voltage Regulator. Generates 5V from 9V battery
- ▶ TSOP – Infra Red (IR) Light Sensor. Converts IR light to electrical voltage pulses
- ▶ 555 – Timer IC operating as Monostable Multivibrator
 - ▶ Converts many voltage pulses into single long voltage pulse
- ▶ 7474 – D FLIP FLOP to store “HIGH” or “LOW” voltage
- ▶ TRANSISTOR – Current Amplifier to drive LED

References

- ▶ www.circuitsgallery.com for the Exhibit 2 Circuit
- ▶ www.buildcircuit.com for the Exhibit 1 Circuit
- ▶ Wikipedia for circuit explanations



GO GREEN